

Hacettepe University Computer Science Department

BBM 233 Logic Design Lab Experiment 5 - Report

Name Surname: Mert Çökelek

ID: 21727082

Email: b21727082@cs.hacettepe.edu.tr

NOTE: My Clock condition is according to "Positive Edge".

The waveform for D Flip Flop:

